



# Physics 421 - Lecture 28

---

Electronics →

RLC →

V

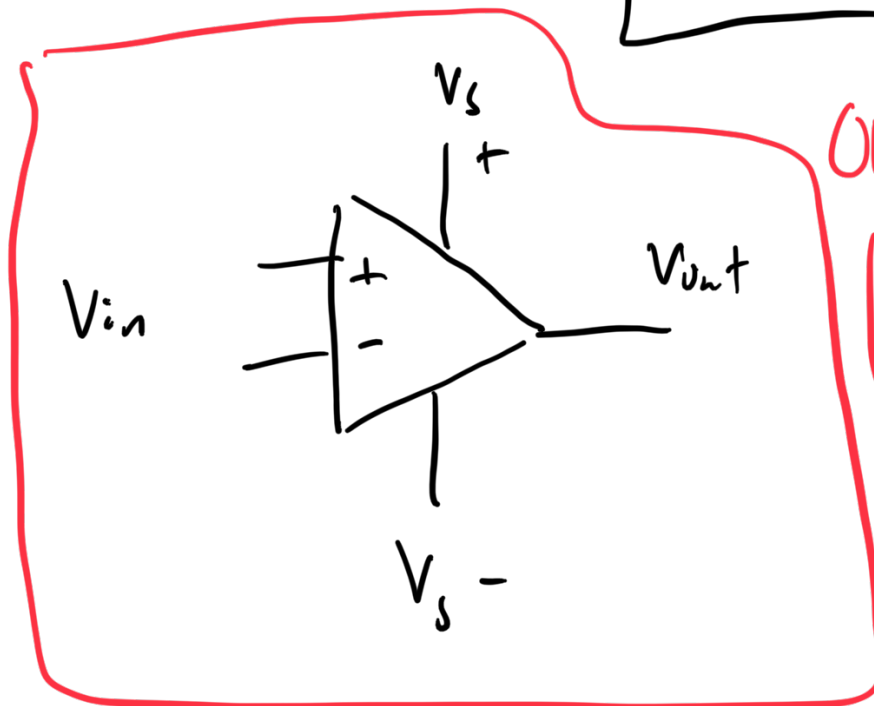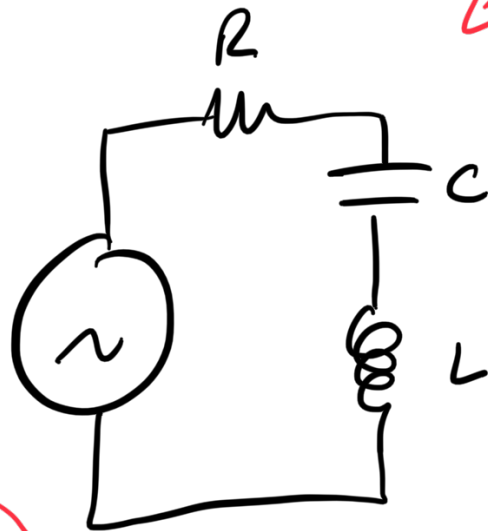


OP AMP

Simulate

DC circuits

$V \rightarrow$  DC battery.

AA

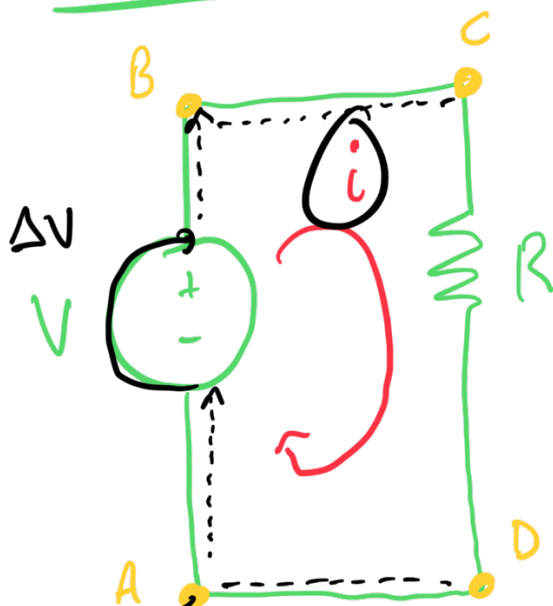

I have no idea!!

$\rightarrow$  Voltage at a point in a circuit  
vs.  $\Delta V$  across an element of the circuit.

$\vec{\mathcal{L}}$  vs.  $\Delta \vec{\mathcal{L}}$

$$V_A = 0$$

$$V_B = V_A + \Delta V_{\text{Battery}} = V_{\text{Battery}}$$

$$V_C = V_B$$

$$V_D = V_A = 0$$

Define the point where  $V=0$ .  
Grounding the circuit.

Ground loops



$$\Delta V_{\text{wires}} \approx 0$$

(include in simulation!)  $R_{\text{wires}} \approx 0 \leftarrow \text{not true!}$

Ohm's Law

Resistors:

$$\Delta V_R = i R$$

textbooks


~~$$V = i R$$~~

$$V_C - V_D = iR$$

$\uparrow \qquad \qquad \uparrow$   
 $V_{\text{Battery}} \quad 0$

$$V_{\text{Battery}} = iR$$

$$i = \frac{V_{\text{Battery}}}{R}$$

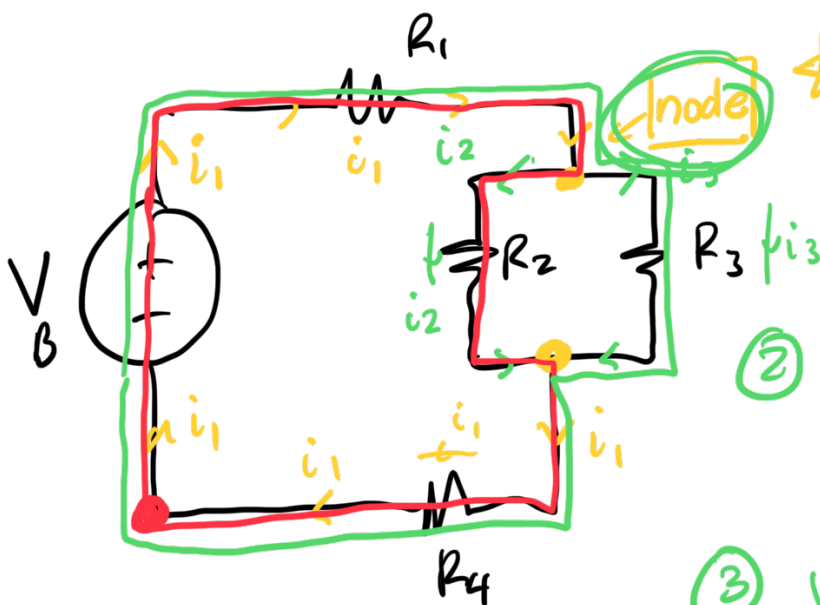

★ super important  
trees / graph

$$\textcircled{2} \quad V_B - i_1 R_1 - i_2 R_2 - i_1 R_4 = 0$$

$$\textcircled{3} \quad V_B - i_1 R_1 - i_3 R_3 - i_1 R_4 = 0$$

"Follow the money"

→ Follow the current.

$$i_1, i_2, i_3$$

Goal

\$\$

3 equations

Nodes

→

Current in = current out

2 nodes

①

$$i_1 = i_2 + i_3$$

1 equation.


$$i_2 + i_3 = i_1$$

$$\# \text{ of node equations} = \frac{\# \text{ nodes}}{2}$$

Closed Loops

$$\sum_{\text{elements}} (\Delta V_i) = 0$$

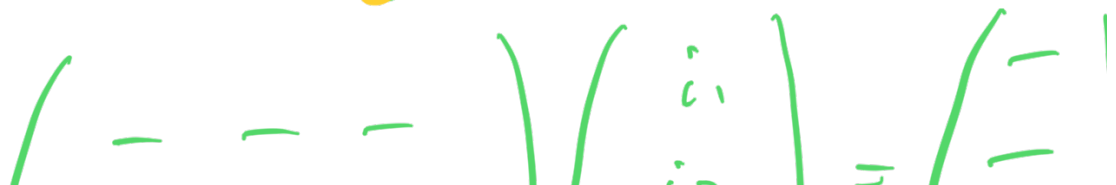✓ Create using ~~graph~~ <sup>graph</sup> theory.



$$\begin{pmatrix} - & - & - \\ - & - & - \end{pmatrix} \begin{pmatrix} i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} - & - & - \\ - & - & - \\ - & - & - \end{pmatrix} \begin{pmatrix} - \\ - \\ - \end{pmatrix}$$

$\begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix}$

Linear Algebra.

---